



Chapter 1

Boolean Logic

These slides support chapter 1 of the book

The Elements of Computing Systems

By Noam Nisan and Shimon Schocken

MIT Press

Chapter 1: Boolean logic



Boolean logic

- Boolean function synthesis
- Hardware description language
- Hardware simulation
- Multi-bit buses
- Project 1 overview

Boolean Values



F

N

0



T

Y

1

Boolean Operations

x And y

$x \wedge y$

x	y	And
0	0	0
0	1	0
1	0	0
1	1	1

x Or y

$x \vee y$

x	y	Or
0	0	0
0	1	1
1	0	1
1	1	1

Not(x)

$\neg x$

x	Not
0	1
1	0

Boolean Expressions

Not(0 Or (1 And 1)) =

Not(0 Or 1) =


Not(1) =

0

Boolean Functions

$$f(x, y, z) = (x \text{ And } y) \text{ Or } (\text{Not}(x) \text{ And } z)$$

x	y	z	f
0	0	0	
0	0	1	1
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

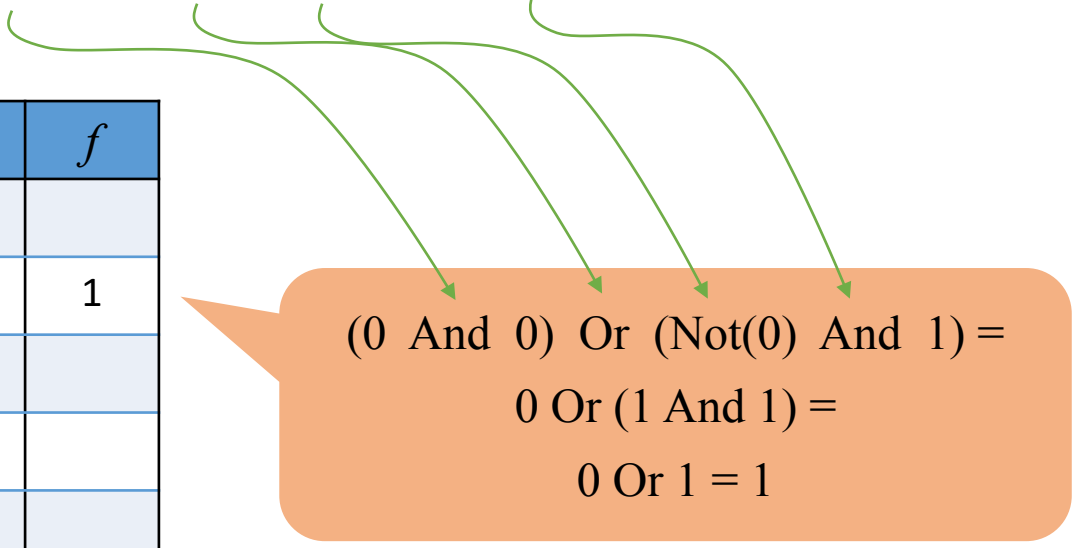

$(0 \text{ And } 0) \text{ Or } (\text{Not}(0) \text{ And } 1) =$
 $0 \text{ Or } (1 \text{ And } 1) =$
 $0 \text{ Or } 1 = 1$

Boolean Functions

$$f(x, y, z) = (x \text{ And } y) \text{ Or } (\text{Not}(x) \text{ And } z)$$

formula

x	y	z	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

truth table

Boolean Identities

- $(x \text{ And } y) = (y \text{ And } x)$
 - $(x \text{ Or } y) = (y \text{ Or } x)$
- } commutative laws
- $(x \text{ And } (y \text{ And } z)) = ((x \text{ And } y) \text{ And } z)$
 - $(x \text{ Or } (y \text{ Or } z)) = ((x \text{ Or } y) \text{ Or } z)$
- } associative laws
- $(x \text{ And } (y \text{ Or } z)) = (x \text{ And } y) \text{ Or } (x \text{ And } z)$
 - $(x \text{ Or } (y \text{ And } z)) = (x \text{ Or } y) \text{ And } (x \text{ Or } z)$
- } distributive laws
- $\text{Not}(x \text{ And } y) = \text{Not}(x) \text{ Or } \text{Not}(y)$
 - $\text{Not}(x \text{ Or } y) = \text{Not}(x) \text{ And } \text{Not}(y)$
- } De Morgan laws

Boolean Algebra

$\text{Not}(\text{Not}(x) \text{ And } \text{Not}(x \text{ Or } y)) =$

De Morgan law

$\text{Not}(\text{Not}(x) \text{ And } (\text{Not}(x) \text{ And } \text{Not}(y))) =$

associative law

$\text{Not}((\text{Not}(x) \text{ And } \text{Not}(x)) \text{ And } \text{Not}(y)) =$

idempotence

$\text{Not}(\text{Not}(x) \text{ And } \text{Not}(y)) =$

De Morgan law

$\text{Not}(\text{Not}(x)) \text{ Or } \text{Not}(\text{Not}(y)) =$

double negation

$x \text{ Or } y$

Boolean Algebra

$\text{Not}(\text{Not}(x) \text{ And } \text{Not}(x \text{ Or } y)) =$



x	y	Or
0	0	0
0	1	1
1	0	1
1	1	1



$x \text{ Or } y$

Chapter 1: Boolean logic



Boolean logic



Boolean function synthesis

- Hardware description language
- Hardware simulation
- Multi-bit buses
- Project 1 overview

Boolean expression $\rightarrow$ truth table

$$f(x, y, z) = (x \text{ And } y) \text{ Or } (\text{Not}(x) \text{ And } z)$$



x	y	z	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Boolean expression $\leftarrow$ truth table

$$f(x, y, z) = (x \text{ And } y) \text{ Or } (\text{Not}(x) \text{ And } z)$$



x	y	z	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

From truth table to a Boolean expression

x	y	z	f
0	0	0	1 1
0	0	1	0 0
0	1	0	1 0
0	1	1	0 0
1	0	0	1 0
1	0	1	0 0
1	1	0	0 0
1	1	1	0 0

(Not(x) And Not(y) And Not(z))

From truth table to a Boolean expression

x	y	z	f
0	0	0	1 0
0	0	1	0 0
0	1	0	1 1
0	1	1	0 0
1	0	0	1 0
1	0	1	0 0
1	1	0	0 0
1	1	1	0 0

(Not(x) And y And Not(z))

From truth table to a Boolean expression

x	y	z	f
0	0	0	1 0
0	0	1	0 0
0	1	0	1 1
0	1	1	0 0
1	0	0	1 1
1	0	1	0 0
1	1	0	0 0
1	1	1	0 0

(x And Not(y) And Not(z))

From truth table to a Boolean expression

x	y	z	f
0	0	0	1 1
0	0	1	0
0	1	0	1 1
0	1	1	0
1	0	0	1 1
1	0	1	0
1	1	0	0
1	1	1	0

(Not(x) And Not(y) And Not(z))

(Not(x) And y And Not(z))

(x And Not(y) And Not(z))

From truth table to a Boolean expression

x	y	z	f
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

(Not(x) And Not(y) And Not(z))

Or

(Not(x) And y And Not(z))

Or

(x And Not(y) And Not(z))

(Not(x) And Not(y) And Not(z)) Or
(Not(x) And y And Not(z)) Or
(x And Not(y) And Not(z)) =

From truth table to a Boolean expression

x	y	z	f
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

(Not(x) And Not(y) And Not(z))

Or

(Not(x) And y And Not(z))

Or

(x And Not(y) And Not(z))

(Not(x) And Not(y) And Not(z)) Or
(Not(x) And y And Not(z)) Or
(x And Not(y) And Not(z)) =

(Not(x) And Not(z)) Or (x And Not(y) And Not(z)) =

(Not(x) And Not(z)) Or (Not(y) And Not(z)) =

Not(z) And (Not(x) Or Not(y))

Theorem

Lemma: Any Boolean function can be represented using an expression containing And, Or And Not operations.

Proof:

Use the truth table to Boolean expression method

Lemma: Any Boolean function can be represented using an expression containing And and Not operations.

Proof:

$$(x \text{ Or } y) = \text{Not}(\text{Not}(x) \text{ And } \text{Not}(y))$$

Can we do better than this?

Nand

x	y	Nand
0	0	1
0	1	1
1	0	1
1	1	0

$$(x \text{ Nand } y) = \text{Not}(x \text{ And } y)$$

Theorem (revisited)

Lemma: Any Boolean function can be represented using an expression containing And, Or And Not operations.

Proof:

Use the truth table to Boolean expression method

Lemma: Any Boolean function can be represented using an expression containing And and Not operations.

Proof:

$$(x \text{ Or } y) = \text{Not}(\text{Not}(x) \text{ And } \text{Not}(y))$$

Theorem: Any Boolean function can be represented using an expression containing Nand operations only.

Proof:

- $\text{Not}(x) = (x \text{ Nand } x)$
- $(x \text{ And } y) = \text{Not}(x \text{ Nand } y)$

Chapter 1: Boolean logic



Boolean logic




Boolean function synthesis





Hardware description language

- Hardware simulation
- Multi-bit buses
- Project 1 overview

Building a logic gate

 

  
outputs 1 if one, and only one, of its inputs, is 1.



The Process:

- ✓ Design the gate architecture
- ✓ Specify the architecture in HDL
- ✓ Test the chip in a hardware simulator
 - Optimize the design
 - Realize the optimized design in silicon.

Design: from requirements to interface

 

outputs 1 if one, and only one, of its inputs, is 1.

a	b	out
0	0	0
0	1	1
1	0	1
1	1	0

Requirement:

Build a gate that delivers this functionality

```
/** Xor gate: out = (a And Not(b)) Or (Not(a) And b) */
```

```
CHIP Xor {  
  IN a, b;  
  OUT out;
```

```
  PARTS:
```


```
    // Implementation missing
```

```
}
```

Gate interface

Expressed as an HDL stub file

 Design: from requirements to gate diagram



outputs 1 if one, and only one, of its inputs, is 1.

a	b	out
0	0	0
0	1	1
1	0	1
1	1	0

Requirement:

Build a gate that delivers this functionality




General idea:

out=1 when:


a And Not(b)

Or

b And Not(a)

 


Design: from gate diagram to HDL

 

```
/** Xor gate: out = (a And Not(b)) Or (Not(a) And b) */  
  
CHIP Xor {  
  IN a, b;  
  OUT out;  
  
  PARTS:  
    // implementation missing  
}
```

Design: from gate diagram to HDL

 

interface {

```
/** Xor gate: out = (a And Not(b)) Or (Not(a) And b) */  
CHIP Xor {  
  IN a, b;  
  OUT out;  
  
  PARTS:  
    Not (in=a, out=nota);  
    Not (in=b, out=notb);  
    And (a=a, b=notb, out=aAndNotb);  
    And (a=nota, b=b, out=notaAndb);  
    Or (a=aAndNotb, b=notaAndb, out=out);  
}
```


implementation {

Other Xor implementations are possible!

HDL: some comments

```
/** Xor gate: out = (a And Not(b)) Or (Not(a) And b) */
```
 
```
CHIP Xor {  
  IN a, b;  
  OUT out;  
  
  PARTS:  
    Not (in=a, out=nota);  
    Not (in=b, out=notb);  
    And (a=a, b=notb, out=aAndNotb);  
    And (a=nota, b=b, out=notaAndb);  
    Or (a=aAndNotb, b=notaAndb, out=out);  
}
```



- HDL is a functional / declarative language
- The order of HDL statements is insignificant
- Before using a chip part, you must know its interface. For example:
`Not(in= ,out=), And(a= ,b= ,out= ), Or(a= ,b= ,out= )`
- Connection patterns like `chipName(a=a,...)` and `chipName(...,out=out)` are common

Hardware description languages

Common HDLs:

- VHDL
- Verilog
- Many more HDLs...

Our HDL

- Similar in spirit to other HDLs
- Minimal and simple
- Provides all you need for this course
- HDL Documentation:



- Textbook / Appendix A
- www.nand2tetris.org / HDL Survival Guide

Chapter 1: Boolean logic



Boolean logic



Boolean function synthesis




Hardware description language



Hardware simulation

- Multi-bit buses
- Project 1 overview

Hardware simulation in a nutshell

 


Simulation options:

- Interactive
- Script-based
- With / without output and compare files

Interactive simulation (using Xor as an example)

Xor.hdl
 
```
CHIP Xor {  
  IN a, b;  
  OUT out;  
  
  PARTS:  
    Not (in=a, out=nota);  
    Not (in=b, out=notb);  
    And (a=a, b=notb, out=aAndNotb);  
    And (a=nota, b=b, out=notaAndb);  
    Or (a=aAndNotb, b=notaAndb, out=out);  
}
```



Simulation process:

- Load the HDL file into the hardware simulator
- Enter values (0's and 1's) into the chip's input pins (e.g. a and b)
- Evaluate the chip's logic
- Inspect the resulting values of:
 - Output pins (e.g. out)
 - Internal pins (e.g. nota, notb, aAndNotb, notaAndb)

Interactive simulation

Hardware Simulator (2.5) - /Users/shimonschocken/Desktop/nand2tetris/week 1/Xor.hdl

File View Run Help

Chip Name: Xor

Input pins

Name	Value
a	0
b	1

Output pins

Name	Value
out	1

HDL

```
CHIP Xor {
  IN a, b;
  OUT out;

  PARTS:
    Not (in=a, out=nota);
    Not (in=b, out=notb);
    And (a=a, b=notb, out=aAndNotb);
    And (a=nota, b=b, out=notaAndb);
    Or (a=aAndNotb, b=notaAndb, out=out);
}
```

Internal pins

Name	Value
nota	1
notb	0
aAndNotb	0
notaAndb	1

1. manipulate input pins

2. evaluate the chip logic

3. inspect output pins

4. inspect internal pins

HDL code

Interactive simulation



Script-based simulation

Xor.hdl

```
CHIP Xor {  
  IN a, b;  
  OUT out;  
  
  PARTS:  
    Not (in=a, out=nota);  
    Not (in=b, out=notb);  
    And (a=a, b=notb, out=aAndNotb);  
    And (a=nota, b=b, out=notaAndb);  
    Or (a=aAndNotb, b=notaAndb, out=out);  
}
```

tested
chip

Xor.tst

```
load Xor.hdl;  
set a 0, set b 0, eval;  
set a 0, set b 1, eval;  
set a 1, set b 0, eval;  
set a 1, set b 1, eval;
```

test script = series of
commands to the simulator

Benefits:

- “Automatic” testing
- Replicable testing

Script-based simulation, with an output file

Xor.hdl

```
CHIP Xor {  
  IN a, b;  
  OUT out;  
  
  PARTS:  
    Not (in=a, out=nota);  
    Not (in=b, out=notb);  
    And (a=a, b=notb, out=aAndNotb);  
    And (a=nota, b=b, out=notaAndb);  
    Or (a=aAndNotb, b=notaAndb, out=out);  
}
```

tested
chip

Xor.tst

```
load Xor.hdl,  
output-file Xor.out,  
output-list a b out;  
set a 0, set b 0, eval, output;  
set a 0, set b 1, eval, output;  
set a 1, set b 0, eval, output;  
set a 1, set b 1, eval, output;
```

test
script

Xor.out

a	b	out
0	0	0
0	1	1
1	0	1
1	1	0

Output File, created
by the test script as a
side-effect of the
simulation process

The logic of a typical test script

- Initialize:
 - Load an HDL file
 - Create an empty output file
 - List the names of the pins whose values will be written to the output file
- Repeat:
 - set – eval - output

Script-based simulation

The screenshot shows the Hardware Simulator (2.5) interface. The title bar indicates the file path: `/Users/shimonschocken/Desktop/nand2tetris/week 1/Xor.hdl`. The menu bar includes File, View, Run, and Help. The toolbar contains various simulation controls, with the 'Run' button (a blue double arrow) circled in blue. A callout bubble points to it with the text 'run the script'. To the right of the 'Run' button, the 'View' dropdown menu is also circled in blue, showing 'Scr...' as the selected option. A callout bubble points to it with the text 'inspect the output file'. Below the toolbar, the 'Chip Name' field is set to 'Xor' and the 'Time' is 0. The 'Input pins' table has two columns: 'Name' and 'Value'. It lists 'a' and 'b'. The 'Output pins' table has two columns: 'Name' and 'Value'. It lists 'out' with a value of 0. The 'HDL' section displays the following code:

```
CHIP Xor {  
  IN a, b;  
  OUT out;  
  
  PARTS:  
    Not (in=a, out=nota);  
    Not (in=b, out=notb);  
    And (a=a, b=notb, out=aAndNotb);  
    And (a=nota, b=b, out=notaAndb);  
    Or (a=aAndNotb, b=notaAndb, out=out);  
}
```

The 'Internal pins' table has two columns: 'Name' and 'Value'. It lists 'nota' (1), 'notb' (1), 'aAndNotb' (0), and 'notaAndb' (0). A callout bubble points to this section with the text 'HDL code'. The 'Script' section on the right contains the following code:

```
load Xor.hdl,  
output-file Xor.out,  
output-list a b out;  
  
set a 0, set b 0, eval, output;  
set a 0, set b 1, eval, output;  
set a 1, set b 0, eval, output;  
set a 1, set b 1, eval, output;
```

A callout bubble points to this section with the text 'test script'.

Script-based simulation




Hardware simulators

- There are many of them!

Our hardware simulator

 - Minimal and simple
- Provides all you need for this course
- Hardware simulator documentation:



www.nand2tetris.org / Hardware Simulator Tutorial

Revisiting script-based simulation with output files

Xor.hdl

```
CHIP Xor {  
  IN a, b;  
  OUT out;  
  
  PARTS:  
    Not (in=a, out=nota);  
    Not (in=b, out=notb);  
    And (a=a, b=notb, out=aAndNotb);  
    And (a=nota, b=b, out=notaAndb);  
    Or (a=aAndNotb, b=notaAndb, out=out);  
}
```

tested
chip

Xor.tst

```
load Xor.hdl,  
output-file Xor.out,  
output-list a b out;  
set a 0, set b 0, eval, output;  
set a 0, set b 1, eval, output;  
set a 1, set b 0, eval, output;  
set a 1, set b 1, eval, output;
```

test
script

Xor.out

a	b	out
0	0	0
0	1	1
1	0	1
1	1	0

Output file, created by the
test script as a side-effect of
the simulation process

Script-based simulation, with compare files

Xor.hdl

```
CHIP Xor {  
  IN a, b;  
  OUT out;  
  
  PARTS:  
    Not (in=a, out=nota);  
    Not (in=b, out=notb);  
    And (a=a, b=notb, out=aAndNotb);  
    And (a=nota, b=b, out=notaAndb);  
    Or (a=aAndNotb, b=notaAndb, out=out);  
}
```

tested
chip

Xor.tst

```
load Xor.hdl,  
output-file Xor.out,  
compare-to Xor.cmp,  
output-list a b out;  
set a 0, set b 0, eval, output;  
set a 0, set b 1, eval, output;  
set a 1, set b 0, eval, output;  
set a 1, set b 1, eval, output;
```

test
script

Xor.cmp

Xor.out

a	b	out
0	0	0
0	1	1
1	0	1
1	1	0

a	b	out
0	0	0
0	1	1
1	0	1
1	1	0

Simulation-with-compare-file logic

- When each output command is executed, the outputted line is compared to the corresponding line in the compare file
- If the two lines are not the same, the simulator throws a comparison error.

Behavioral simulation

Xor.hdl

```
CHIP Xor {  
  IN a, b;  
  OUT out;  
  
  BUILTIN Xor  
  // Built-in chip implementation,  
  // can execute in the hardware  
  // simulator like any other chip.  
}
```

built-in chip
implementation

Xor.tst

```
load Xor.hdl,  
output-file Xor.out,  
output-list a b out;  
  
set a 0, set b 0, eval, output;  
set a 0, set b 1, eval, output;  
set a 1, set b 0, eval, output;  
set a 1, set b 1, eval, output;
```

test
script

Behavioral simulation:

- The chip logic (abstraction) can be implemented in some high-level language
- Enables high-level planning and testing of a hardware architecture before writing any HDL code.

Xor.out

a	b	out
0	0	0
0	1	1
1	0	1
1	1	0

Xor.cmp

a	b	out
0	0	0
0	1	1
1	0	1
1	1	0

Hardware construction projects

- The players (first approximation):
 - System architects
 - Developers
- The system architect decides which chips are needed
- For each chip, the architect creates
 - A chip API
 - A test script
 - A compare file
- Given these resources, the developers can build the chips.

The developer's view (of, say, a Xor gate)

Xor.hdl

```
/** returns 1 if (a != b) */  
  
CHIP Xor {  
    IN a, b;  
    OUT out;  
  
    PARTS:  
        // Implementation missing  
}
```

stub
file

Xor.tst

```
load Xor.hdl,  
output-file Xor.out,  
compare-to Xor.cmp  
output-list a b out;  
set a 0, set b 0, eval, output;  
set a 0, set b 1, eval, output;  
set a 1, set b 0, eval, output;  
set a 1, set b 1, eval, output;
```

test
script

- Taken together, the three files provide a convenient specification of:
 - The chip interface (.hdl)
 - What the chip is supposed to do (.cmp)
 - How to test the chip (.tst)
- The developer's task:
implement the chip, using these resources.

Xor.cmp

a	b	out
0	0	0
0	1	1
1	0	1
1	1	0

compare
file

Chapter 1: Boolean logic



Boolean logic



Boolean function synthesis



Hardware description language



Hardware simulation



Multi-bit buses

- Project 1 overview

Arrays of Bits

- Sometimes we wish to manipulate an array of bits as one group
- It's convenient to think about such a group of bits as a single entity, sometime termed “bus”
- HDLs usually provide notation and means for handling buses.

Example: adding 16-bit integers


```
/*  
 * Adds two 16-bit values.  
 */
```

```
CHIP Add16 {  
  IN a[16], b[16];  
  OUT out[16];
```

PARTS:

...

```
}
```

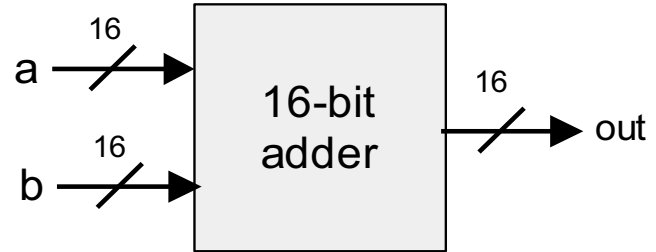

```
/*  
 * Adds three 16-bit inputs.  
 */
```

```
CHIP Add3Way16 {  
  IN first[16], second[16], third[16];  
  OUT out[16];
```

PARTS:

```
Add16(a=first, b=second, out=temp);
```

```
Add16(a=temp, b=third, out=out);
```

```
}
```

Working with individual bits within buses

```
/*  
 * 4-way And: Ands 4 bits.  
 */  
CHIP And4Way {  
    IN a[4];  
    OUT out;  
  
    PARTS:  
        And(a=a[0], b=a[1], out=t01);  
        And(a=t01, b=a[2], out=t012);  
        And(a=t012, b=a[3], out=out);  
}
```

Working with individual bits within buses

```
/*  
 * Bit-wise And of two 4-bit inputs  
 */  
CHIP And4 {  
    IN a[4], b[4];  
    OUT out[4];  
  
    PARTS:  
        And(a=a[0], b=b[0], out=out[0]);  
        And(a=a[1], b=b[1], out=out[1]);  
        And(a=a[2], b=b[2], out=out[2]);  
        And(a=a[3], b=b[3], out=out[3]);  
}
```

Sub-buses

Buses can be composed from (and decomposed into) sub-buses

```
...  
IN lsb[8], msb[8], ...  
...  
Add16(a[0..7]=lsb, a[8..15]=msb, b=..., out=...);  
Add16(..., out[0..3]=t1, out[4..15]=t2);
```

Some syntactic choices of our HDL

- buses are indexed right to left: if `foo` is a 16-bit bus, then `foo[0]` is the right-most bit, and `foo[15]` is the left-most bit
- overlaps of sub-buses are allowed in output buses of parts
- width of internal pin buses is deduced automatically
- The `false` and `true` constants may be used as buses of any width.

Chapter 1: Boolean logic



Boolean logic



Boolean function synthesis



Hardware description language



Hardware simulation




Multi-bit buses



Project 1 overview

Nand to Tetris course methodology

 

Project 1: the first step

Project 1

Given: Nand

Goal: Build the following gates:

Elementary logic gates

- Not
- And
- Or
- Xor
- Mux ←
- DMux ←

16-bit variants

- Not16
- And16 ←
- Or16
- Mux16

Multi-way variants

- Or8Way
- Mux4Way16 ←
- Mux8Way16
- DMux4Way
- DMux8Way

Why these 15 particular gates?

- Commonly used gates
- Comprise all the elementary logic gates needed to build our computer.

Project 1

Given: Nand

Goal: Build the following gates:

Elementary logic gates

- Not
- And
- Or
- Xor
- Mux 
- DMux 


16-bit variants

- Not16
- And16
- Or16
- Mux16

Multi-way variants

- Or8Way
- Mux4Way16
- Mux8Way16
- DMux4Way
- DMux8Way

Multiplexor

 

```
if (sel==0)
    out=a
else
    out=b
```


a	b	sel	out
0	0	0	0
0	1	0	0
1	0	0	1
1	1	0	1
0	0	1	0
0	1	1	1
1	0	1	0
1	1	1	1

sel	out
0	a
1	b

abbreviated
truth table

- A 2-way multiplexor enables selecting, and outputting, one of two possible inputs
- Widely used in:
 - Digital design
 - Communications networks

 Example: using mux logic to build a programmable gate




```
if (sel==0)
    out = (a And b)
else
    out = (a Or b)
```

a	b	sel	out
0	0	0	0
0	1	0	0
1	0	0	0
1	1	0	1
0	0	1	0
0	1	1	1
1	0	1	1
1	1	1	1

When sel==0
the gate acts like
an And gate

 When sel==1
the gate acts like
an Or gate




Mux.hdl

```
CHIP AndMuxOr {
    IN a, b, sel;
    OUT out;

    PARTS:
        And (a=a, b=b, out=andOut);
        Or (a=a, b=b, out=orOut);
        Mux (a=andOut, b=orOut, sel=sel, out=out);
}
```

Multiplexor implementation

 

```
if (sel==0)
  out=a
else
  out=b
```

sel	out
0	a
1	b

Mux.hdl


```
CHIP Mux {
  IN a, b, sel;
  OUT out;

  PARTS:
    // Put your code here:
}
```

Implementation tip:

Can be implemented with
And, Or, and Not gates

Demultiplexor

 

```
if (sel==0)
    {a,b}={in,0}
else
    {a,b}={0,in}
```

in	sel	a	b
0	0	0	0
0	1	0	0
1	0	1	0
1	1	0	1


- Acts like the “inverse” of a multiplexor
- Distributes the single input value into one of two possible destinations

DMux.hdl

```
CHIP DMux {
    IN in, sel;
    OUT a, b;

    PARTS:
        // Put your code here:
}
```

 Example: Multiplexing / demultiplexing in communications networks



- Each `sel` bit is connected to an oscillator that produces a repetitive train of alternating 0 and 1 signals
- Enables transmitting multiple messages on a single, shared communications line
- A common use of multiplexing / demultiplexing logic
- Unrelated to this course.

Project 1

Elementary logic gates

- Not
- And
- Or
- Xor
- Mux
- DMux

16-bit variants


- Not16
- And16
- Or16
- Mux16



Multi-way variants

- Or8Way
- Mux4Way16
- Mux8Way16
- DMux4Way
- DMux8Way

And16

 

```
CHIP And16 {  
    IN a[16], b[16];  
    OUT out[16];  
  
    PARTS:  
    // Put your code here:  
}
```

a = 1 0 1 0 1 0 1 1 0 1 0 1 1 1 0 0
b = 0 0 1 0 1 1 0 1 0 0 1 0 1 0 1 0

out = 0 0 1 0 1 0 0 1 0 0 0 0 1 0 0 0

- A straightforward 16-bit extension of the elementary And gate
(See previous slides on working with multi-bit buses)

Project 1

Elementary logic gates

- Not
- And
- Or
- Xor
- Mux
- DMux


16-bit variants

- Not16
- And16
- Or16
- Mux16

Multi-way variants

- Or8Way
- Mux4Way16 
- Mux8Way16
- DMux4Way
- DMux8Way

16-bit, 4-way multiplexor

 

sel[1]]	sel[0]	out
0	0	a
0	1	b
1	0	c
1	1	d

Mux4Way16.hdl

```
CHIP Mux4Way16 {  
  IN a[16], b[16], c[16], d[16],  
      sel[2];  
  OUT out[16];  
  
  PARTS:  
    // Put your code here:  
}
```

Implementation tip:

Can be built from several Mux16 gates

Project 1

Given: Nand

Goal: Build the following gates:

Elementary logic gates

- Not
- And
- Or
- Xor
- Mux
- DMux

16-bit variants

- Not16
- And16
- Or16
- Mux16


Multi-way variants

- Or8Way
- Mux4Way16
- Mux8Way16
- DMux4Way
- DMux8Way



So how to actually build
these gates?

 Chip building materials (using Xor as an example)



outputs 1 if $a \neq b$

Xor.cmp

a	b	out
0	0	0
0	1	1
1	0	1
1	1	0

The contract:

When running your Xor.hdl on the supplied Xor.tst, your Xor.out should be the same as the supplied Xor.cmp

Xor.hdl

```
CHIP Xor {  
    IN  a, b;  
    OUT out;  
  
    PARTS:  
    // Put your code here.  
}
```

Xor.tst

```
load Xor.hdl,  
output-file Xor.out,  
compare-to Xor.cmp,  
output-list a b out;  
set a 0, set b 0, eval, output;  
set a 0, set b 1, eval, output;  
set a 1, set b 0, eval, output;  
set a 1, set b 1, eval, output;
```

Project 1 Resources

From NAND to Tetris
Building a Modern Computer From First Principles

www.nand2tetris.org



Home
Prerequisites
Syllabus

Course

Book
Software
Terms
Papers
Talks
Cool Stuff
About
Team
Q&A

Project 1: Elementary Logic Gates

Background

A typical computer architecture is based on a set of elementary logic gates like And, Or, Mux, etc., as well as their bit-wise versions And16, Or16, Mux16, etc. (assuming a 16-bit machine). This project engages you in the construction of a typical set of basic logic gates. These gates form the elementary building blocks from which more complex chips will be later constructed.

Objective

Build all the logic gates described in Chapter 1 (see list below), yielding a basic chip-set. The only building blocks that you can use in this project are primitive Nand gates and the composite gates that you will gradually build on top of them.

Chips


Chip (HDL)	Description	Test Script	Compare File
Nand	Nand gate (primitive)		
Not	Not gate	Not.tst	Not.cmp
And	And gate	And.tst	And.cmp
Or	Or gate	Or.tst	Or.cmp
Xor	Xor gate	Xor.tst	Xor.cmp
Mux	Mux gate	Mux.tst	Mux.cmp
DMux	DMux gate	DMux.tst	DMux.cmp
Not16	16-bit Not	Not16.tst	Not16.cmp
And16	16-bit And	And16.tst	And16.cmp
Or16	16-bit Or	Or16.tst	Or16.cmp
Mux16	16-bit multiplexor	Mux16.tst	Mux16.cmp

All the necessary project 1 files
are available in:
[nand2tetris/projects/01](#)

More resources

- Text editor (for writing your HDL files)
 - HDL Survival Guide
 - Hardware Simulator Tutorial
 - nand2tetris Q&A forum
- } All available in: www.nand2tetris.org

Hack chipset API

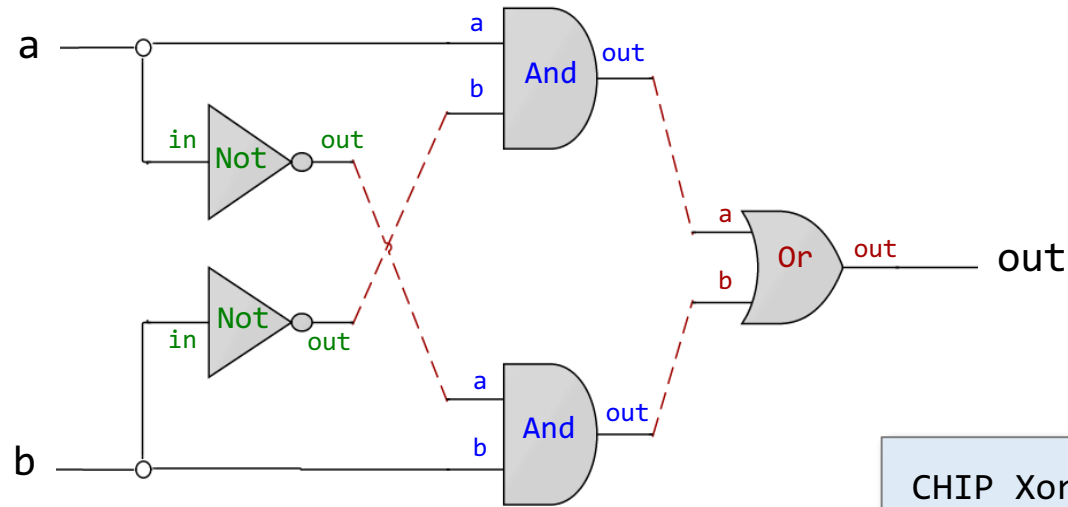

When deciding to use some chip-parts, how do I know the names of their input and output pins?

```
CHIP Xor {  
  IN a, b;  
  OUT out;  
  
  PARTS:  
    Not (in= , out=);  
    Not (in= , out=);  
    And (a= , b= , out=);  
    And (a= , b=b , out=);  
    Or (a= , b= , out=);  
}
```


Hack chipset API

```
Add16 (a= ,b= ,out= );
ALU (x= ,y= ,zx= ,nx= ,zy= ,ny= ,f= ,no= ,out= ,zr= ,ng= );
And16 (a= ,b= ,out= );
And (a= ,b= ,out= );
Aregister (in= ,load= ,out= );
Bit (in= ,load= ,out= );
CPU (inM= ,instruction= ,reset= ,outM= );
DFF (in= ,out= );
DMux4Way (in= ,sel= ,a= ,b= ,c= ,d= );
DMux8Way (in= ,sel= ,a= ,b= ,c= ,d= );
Dmux (in= ,sel= ,a= ,b= );
Dregister (in= ,load= ,out= );
FullAdder (a= ,b= ,c= ,sum= ,carry= );
HalfAdder (a= ,b= ,sum= , carry= );
Inc16 (in= ,out= );
Keyboard (out= );
Memory (in= ,load= ,address= ,out= );
Mux16 (a= ,b= ,sel= ,out= );
Mux4Way16 (a= ,b= ,c= ,d= ,sel= ,out= );
Mux8Way16 (a= ,b= ,c= ,d= ,e= ,f= ,g= );
Mux8Way (a= ,b= ,c= ,d= ,e= ,f= ,g= ,h= ,sel= ,out= );
Mux (a= ,b= ,sel= ,out= );
Nand (a= ,b= ,out= );
Not16 (in= ,out= );
Not (in= ,out= );
Or16 (a= ,b= ,out= );
Or8Way (in= ,out= );
Or (a= ,b= ,out= );
PC (in= ,load= ,inc= ,reset= ,out= );
PCLoadLogic (cinstr= ,j1= ,j2= ,j3= ,load= ,inc= );
RAM16K (in= ,load= ,address= ,out= );
RAM4K (in= ,load= ,address= ,out= );
RAM512 (in= ,load= ,address= ,out= );
RAM64 (in= ,load= ,address= ,out= );
RAM8 (in= ,load= ,address= ,out= );
Register (in= ,load= ,out= );
ROM32K (address= ,out= );
Screen (in= ,load= ,address= ,out= );
Xor (a= ,b= ,out= );
```



(see *HDL Survival Guide* @ www.nand2tetris.org)

Built-in chips
 
```
CHIP Foo {  
    IN ...;  
    OUT ...;  
  
    PARTS:  
    ...  
    Mux16(...)   
    ...  
}
```

Q: What happens if there is no Mux16.hdl file in the current directory?

A: The simulator invokes, and evaluates, the built-in version of Mux16 (if such exists).

- The supplied simulator software features built-in chip implementations of all the chips in the Hack chip set
- If you don't implement some chips from the Hack chipset, you can still use them as chip-parts of other chips:
 - Just rename their given stub files to, say, Mux16.hdl1
 - This will cause the simulator to use the built-in chip implementation.

Best practice advice

- Try to implement the chips in the given order
- If you don't implement some chips, you can still use them as chip-parts in other chips (the built-in implementations will kick in)
- You can invent new, “helper chips”; however, this is not required: you can build any chip using previously-built chips only
- Strive to use as few chip-parts as possible.

Chapter 1: Boolean logic

- ✓ Boolean logic
- ✓ Boolean function synthesis
- ✓ Hardware description language
- ✓ Hardware simulation
- ✓ Multi-bit buses
- ✓ Project 1 overview



Chapter 1

Boolean Logic

These slides support chapter 1 of the book

The Elements of Computing Systems

By Noam Nisan and Shimon Schocken

MIT Press